

CSEN102 – Introduction to Computer Science

Lecture 9: Boolean Logic

Prof. Dr. Slim Abdennadher

Dr. Aysha Alsafty

`slim.abdennadher@guc.edu.eg,`

`aysha.alsafty@guc.edu.eg`

German University Cairo, Department of Media Engineering and Technology

18.12.2016 - 22.12 2016

Synopsis

Test your understanding. . .


- What is the **range** of a n -bit unsigned binary integer?
from 0 to $2^n - 1$
- What is the **range** of an n -digit unsigned base- b integer?
from 0 to $b^n - 1$
- What is the **range** of a n -bit binary two's complement integer?
from -2^{n-1} to $2^{n-1} - 1$
- What is the **advantage** of the **two's complement representation** for negative numerals over others?
 - Addition of negative numbers is exactly the same as with positive numbers
 - It uses the full capacity of an n -bit numeral
- How do I **convert** a positive binary into the corresponding **two's complement negative**?
 - Flip every bit
 - Add 1

Synopsis

As promised:

The idea of the two's complement addition

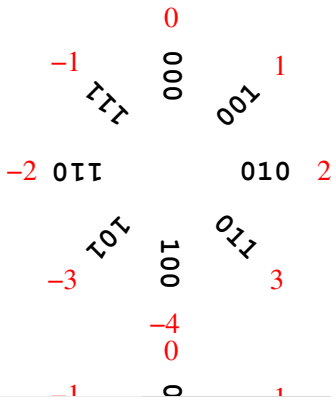- For the example, we consider **3-bit** two's complement integers
- We add 3 and -2



Synopsis

Test your understanding. . .

- Define the normalized scientific floating-point notation
 - The numbers are represented as $\pm \text{mantissa} \times \text{base}^{\pm \text{exponent}}$
 - Normalized means that the most significant bit is right of the fraction-point.
- Assume the following encoding for a 16-bit normalized binary floating point:

Sign of mantissa 1 bit	Mantissa 9 bits	Sign of exponent 1 bit	Exponent 5 bits
---------------------------	--------------------	---------------------------	--------------------

How do you represent the number 10.01011?

0100101100100010


Be prepared to explain why!

New chapter

Boolean Logic

Boolean logic

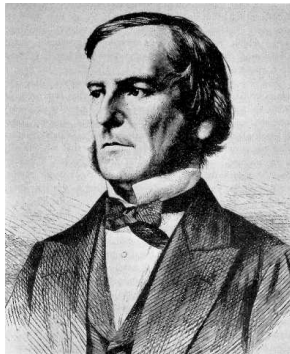- **Boolean logic** is a branch of mathematics that deals with rules for manipulating two logical values **true** and **false**.
- Named after **George Boole** (1815-1864)
- Why is Boolean logic so relevant to computers?
 - Straightforward mapping to binary digits!
 - **0** is **false**
 - **1** is **true**



Boolean operations

- **Boolean expression** is any expression that evaluates to either true or false (ex: $X = 5$, $2 < 4$).
- Boolean expressions are widely used in programming. They are formed from **variables** and **operations**.
- **Variables** are designated by letters (e. g., a , b , c , x , y , ...). Each variable takes only one of 2 values: **0** or **1**.
- The three **basic operations** are:
 - AND** **product**, **conjunction** of two inputs
Expression: xy or $x * y$ or $x \wedge y$
 - OR** **sum**, **disjunction** of two inputs
Expression: $x + y$ or $x \vee y$
 - NOT** **negation**, **complement** of one input
Expression: x' or \bar{x} or $\neg x$

Truth tables for the basic operations

Truth tables are useful as **definition** and **proof-tool** for boolean operators:

AND (conjunction)

x	y	$x * y$
0	0	0
0	1	0
1	0	0
1	1	1

OR (disjunction)

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT (complement)

x	$\neg x$
0	1
1	0

Logical AND

- The **AND** takes two expressions as input (e. g., A and B)
- It evaluates to **TRUE** only if both expressions are TRUE
- Written as $A * B$ or AB

Example

- A = It is sunny
- B = I am in vacation
- $(A * B)$ = It is sunny **AND** I am in vacation

A	B	$A * B$
0	0	0
0	1	0
1	0	0
1	1	1

Logical OR

- The **OR** takes two expressions as input, (e. g., A and B)
- It evaluates to **TRUE** if either A is TRUE or B is TRUE or both expressions are TRUE
- Written as $A + B$

Example

- A = It is sunny
- B = I am in vacation
- $(A + B)$ = It is sunny **OR** I am in vacation **OR** both

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

Logical NOT

- The **NOT** takes one expression as input, (e. g., A)
- It evaluates to **TRUE** if A is FALSE (used to invert a meaning)
- Written as A'

Example

- A = It is sunny
- A' = It is not sunny

A	A'
0	1
1	0

Boolean algebra

Boolean expressions are defined through an **algebra**.

A Boolean Algebra requires:

- A set of values with at least two elements, denoted **0** and **1**
- Two binary operations **+** and *****
- A unary operation **'**

Boolean algebra

A Boolean Algebra must satisfy these axioms:

$x + 0 = x$	$x * 1 = x$	
$x + 1 = 1$	$x * 0 = 0$	
$x + x = x$	$x * x = x$	
$x + x' = 1$	$x * x' = 0$	
$(x')' = x$		
$x + y = y + x$	$xy = yx$	Commutativity
$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$	Associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	Distributivity
$(x + y)' = x'y'$	$(xy)' = x' + y'$	DeMorgan's Law

Boolean algebra

Note:

- The **AND** and **OR** are **similar** to multiplication and addition.
 - **AND** yields the same results as multiplication for the values 0 and 1.
 - **OR** is almost the same as addition, expect for the case $1 + 1$.

x	y	$x * y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

- This explains why we borrow the arithmetic symbols $*$, $+$, 0 and 1 for Boolean operations.
- But there are **important differences** too.
 - There are a finite number of Boolean values: 0 and 1.
 - **OR** is not quite the same as addition.
 - **NOT** is a new operation.

Boolean algebra

A Boolean Algebra must satisfy these axioms:

$x + 0 = x$	$x * 1 = x$	
$x + 1 = 1$	$x * 0 = 0$	
$x + x = x$	$x * x = x$	
$x + x' = 1$	$x * x' = 0$	
$(x')' = x$		
$x + y = y + x$	$xy = yx$	Commutativity
$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$	Associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	Distributivity
$(x + y)' = x'y'$	$(xy)' = x' + y'$	DeMorgan's Law
$x + 0 = x$	$x * 1 = x$	
$x + 1 = 1$	$x * 0 = 0$	
$x + x = x$	$x * x = x$	
$x + x' = 1$	$x * x' = 0$	
$(x')' = x$		
$x + y = y + x$	$xy = yx$	Commutativity
$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$	Associativity

Boolean algebra

Think about English examples

- “It is snowing or it is not snowing” is always true ($x + x' = 1$).
- “It is snowing and it is not snowing” can never be true ($x * x' = 0$).
- “I am not not handsome” means that “I am handsome” ($(x')' = x$).

DeMorgan's laws

These laws explain how to complement arbitrary expressions.

- “I am not rich-or-famous” means that “I am not rich and I am not famous”
- “I am not old-and-bald” means that “I am not old or I am not bald”.
But I could be (1) young and bald, or (2) young and hairy or (3) old and hairy.

Boolean expressions

- Using the basic operations, we can form more complex expressions

$$f(x, y, z) = (x + y')z + x'$$

- Terminology and notation

- f is the **name** of the function
- x, y and z are **input variables**, which range over 0 and 1.
- A **literal** is any occurrence of an input or its complement.

- Precedences are important.

- NOT** has the highest precedence, followed by **AND**, and then **OR**.
- Fully parenthesized, the expression above would be written:

$$f(x, y, z) = (((x + (y')) * z) + x')$$

Truth tables

- A **truth table** represents **all possible values** of an expression given the possible values of its inputs.
- How do we **build** a truth table?
 - 1 Create columns for all variables
 - 2 Determine the number of rows needed (how many rows should appear?)
 - For n variables, 2^n rows.
 - 3 Define all possible values for the inputs starting from all **0's** to all **1's** (e. g., for 3 input variables from 000 to 111)
 - 4 Find the value of the expression for each input value and fill in the table.

Truth tables – Example

Example

$$f(x, y, z) = (x + y')z + x'$$

x	y	z	$f(x, y, z)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

How to translate a truth table to a boolean expression?

Idea

A	B	Output
0	0	0
0	1	0
1	0	1
1	1	0

- **Sum-of-Products-Algorithm:**

- Form AND terms for each row that has 1 as the expected
 - use x if it corresponds to $x = 1$
 - use x' if it corresponds to $x = 0$
- OR the terms together
- The resulting expression then represents the complete functionality of the truth table.

Sum-of-Products-Algorithm – Example

x	y	z	$f(x, y, z)$	
0	0	0	1	←
0	0	1	1	←
0	1	0	1	←
0	1	1	1	←
1	0	0	0	
1	0	1	1	←
1	1	0	0	
1	1	1	1	←

$$f(x, y, z) = x'y'z' + x'y'z + x'yz' + x'yz + xy'z + xyz$$

Circuits

Encoding boolean logic in hardware

Expressions and circuits


- A **circuit** is a **network of gates** that implements one or more boolean functions.
- We can build a circuit for any Boolean expression by **connecting primitive logic gates** in the correct order.
- Notice that the order of operations is explicit in the circuit.

Primitive logic gates

- A **gate** is an electronic device that operates on a collection of binary inputs to produce a binary output.
- Each basic operation can be **implemented in hardware** with a logic gate.

AND (conjunction)


x	y	$x * y$
0	0	0
0	1	0
1	0	0
1	1	1

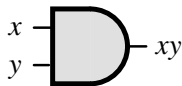

AND

OR (disjunction)


x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

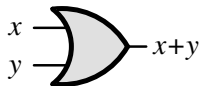

OR

NOT (complement)

x	$\neg x$
0	1
1	0

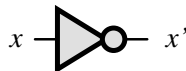

NOT

Encoding boolean logic in hardware

Example


● Truth table:

X	Y	Z	S
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

● Expression:

$$f(x, y, z) = x' * y * z + x * y * z'$$

● Circuit:

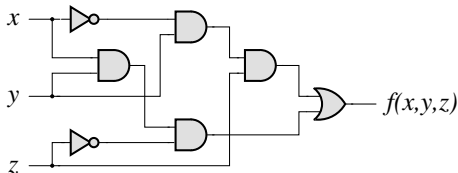

Equivalence proof with truth tables

- Two expressions are **equivalent** iff they always produce the same results for the same inputs

Example $((x + y)' = x'y')$

x	y	$x + y$	$(x + y)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

x	y	x'	y'	$x'y'$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0